

EEL 4837

Programming for Electrical Engineers II

Ivan Ruchkin

Assistant Professor

Department of Electrical and Computer Engineering

University of Florida at Gainesville

iruchkin@ece.ufl.edu

<http://ivan.ece.ufl.edu>


Excursion 1 – Circuit Analysis Tool

Readings:

- Excursion 1 Description


Electronic Circuit

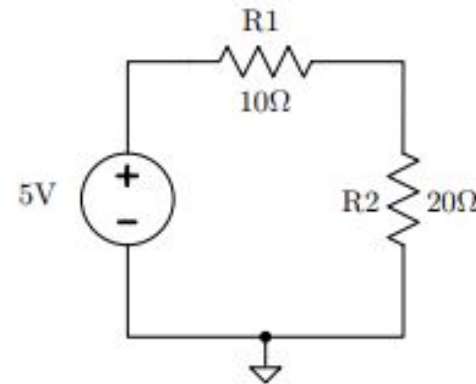- **Electronic circuit:** a collection of interconnected electronic components
- A circuit has a well-defined deterministic functionality when running:
 - Voltage sources
 - Current sources
 - Resistors
 - Inductors
 - Capacitors
 - Diodes
 - Transistors
 - ...



Electronic Circuit (cont.)

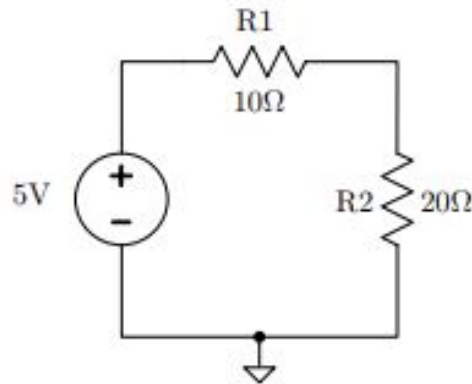- The functionality of a circuit is fully characterized by:
 - The **current** through each component
 - The **voltage drop/rise** through each component
 - The **voltage potential** at each of the interconnections relative to an **arbitrary ground node**




Circuit Analysis

- **Circuit analysis:** a sequence of methods to answer some questions about circuit
 - E.g., what is the voltage drop/rise across a resistor?
- To do that, we may need:
 - Measuring tools
 - E.g., Galvanometer, voltmeter, ohmmeter, etc
 - Theories
 - E.g., Ohm's Law, Voltage Law, Current Law, etc

Circuit Simulation


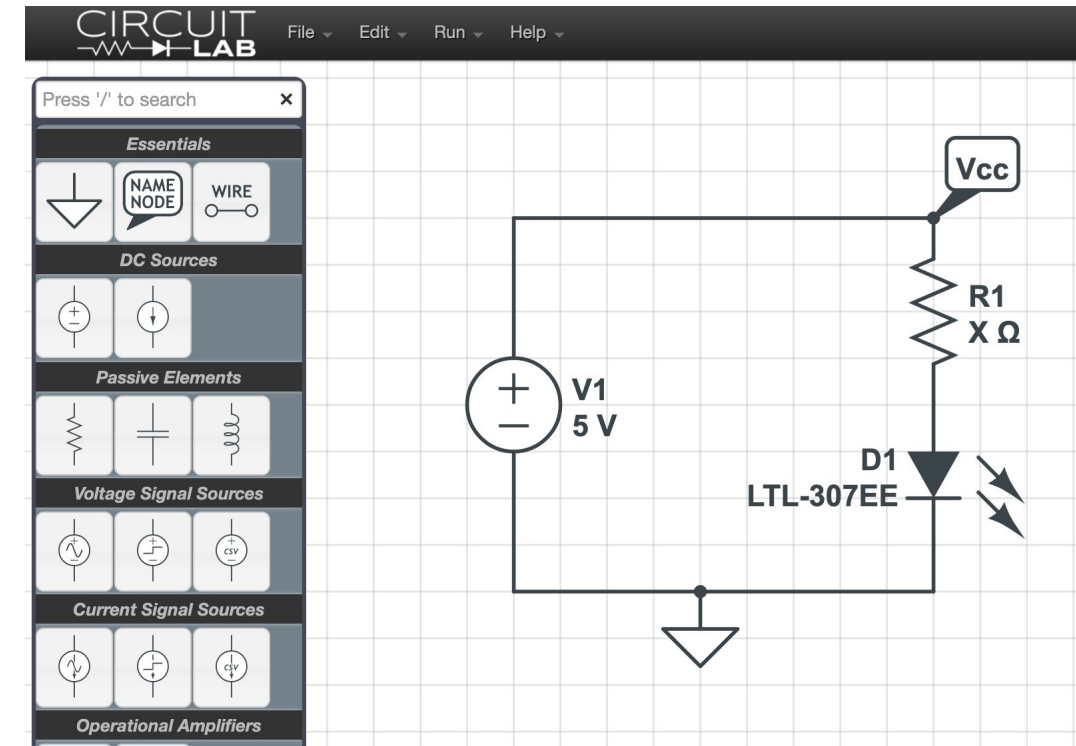
- **Circuit simulation:** a technique to check and verify the design of circuits prior to manufacturing and deployment.
- Almost replaced physical prototype
- What can we do with simulation?
 - Model a linear circuit with a single matrix algebraic equation



From: [CircuitLab](#)



Schematic Diagrams and Digraphs

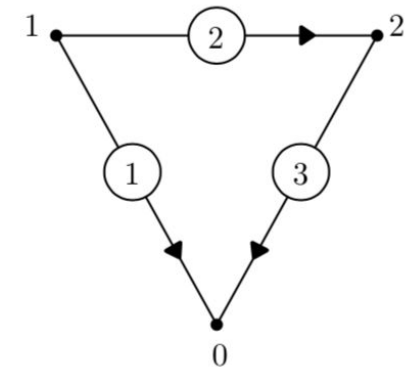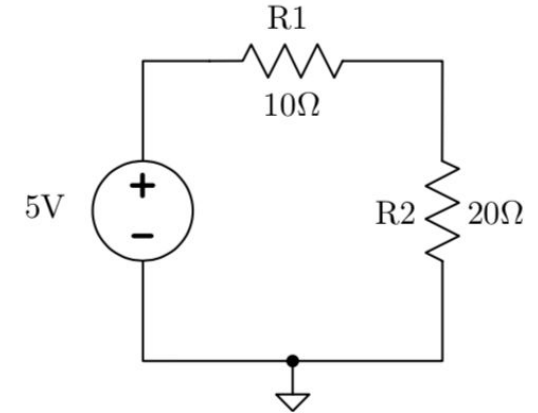- **Schematic diagram:** a graphical representation of an electrical circuit
- **Directed graph (digraph):** can represent a circuit more abstractly (from graph theory)



Circuit Netlist

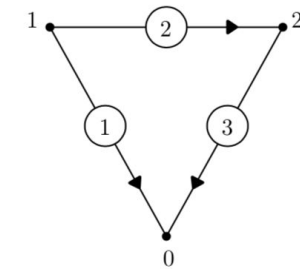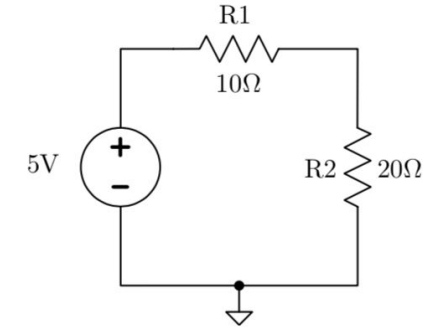
- **Netlist:** describes the connectivity of an electronic circuit
- It consists of:
 - A list of **electronic components**
 - A list of **nodes** they are connected to
- **Format:**
 - Branch label
 - First character indicates component type
 - Source node label
 - Destination node label
 - Numeric component value



V1	1	0	5
R1	1	2	10
R2	2	0	20

Circuit Netlist Conventions

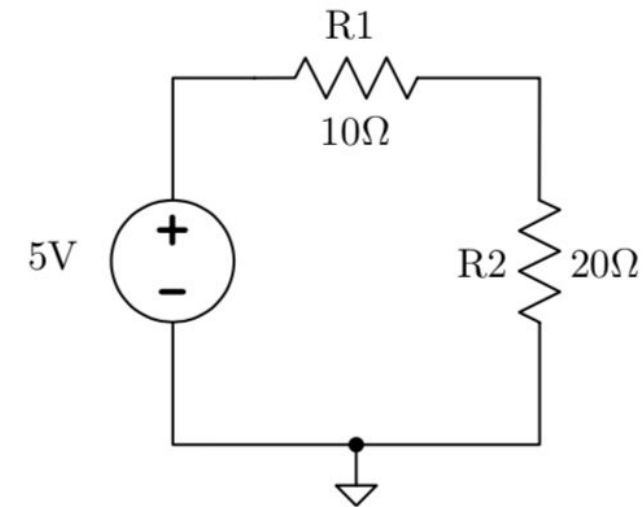
- Ground node is always labeled as 0, while other node can be labeled in any order
- Use positive numeric values
 - Current travels from source to destination.
 - Voltage drops from source to destination.



V1	1	0	5
R1	1	2	10
R2	2	0	20

Data Structure for Circuits

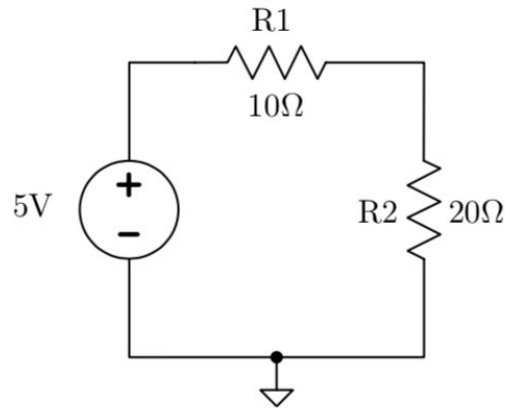- How can we represent a circuit in a program?



Circuit
Diagram



V1	1	0	5
R1	1	2	10
R2	2	0	20

Netlist



$$\begin{bmatrix} \mathbf{0} & \mathbf{0} & \mathbf{A} \\ -\mathbf{A}^T & \mathbf{1} & \mathbf{0} \\ \mathbf{0} & \mathbf{M} & \mathbf{N} \end{bmatrix} \begin{bmatrix} \mathbf{e} \\ \mathbf{v} \\ \mathbf{i} \end{bmatrix} = \begin{bmatrix} \mathbf{0} \\ \mathbf{0} \\ \mathbf{u}_s \end{bmatrix}$$

Matrix

Excursion 1 Goal


- An elementary interactive **circuit analysis tool** to:
 - Read a circuit from a file
 - Compute the currents and voltages across different components
 - Outputs them into a file
- You can assume that the given circuits only contain:
 - Voltage sources
 - Resistors

Steps Overview

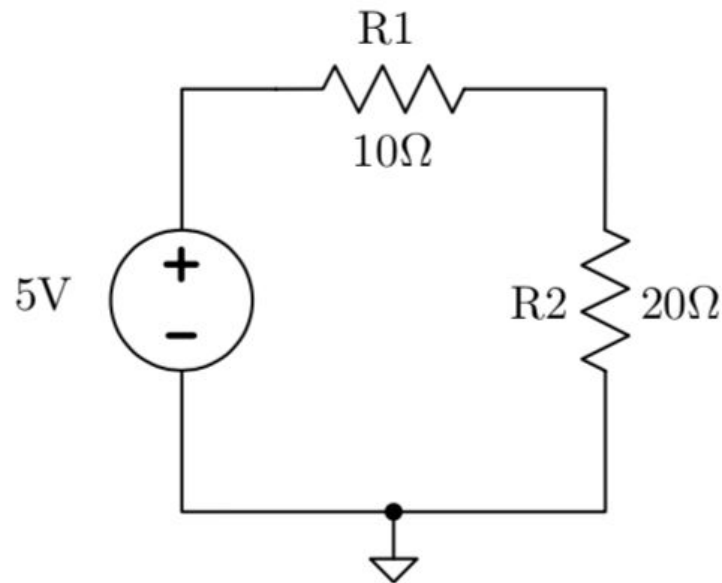1. Read a netlist as input to represent a circuit
2. Use KCL, KVL, and Ohm's law to construct three matrix equations
3. Combine all the matrix equations to solve all the unknown parameters (**\mathbf{e}** , **\mathbf{v}** , **\mathbf{i}** of each part)
4. Output voltages and currents

Step 1: Read a Netlist

- Based on a circuit diagram, create its corresponding *netlist* as input
 - You'll be reading a netlist from a text file



V1	1	0	5
R1	1	2	10
R2	2	0	20

Step 2: From Netlist to Matrix



- Represent the netlist with an *incidence matrix*

V1	1	0	5
R1	1	2	10
R2	2	0	20



$$A_a = \begin{matrix} & \begin{matrix} n_0 \\ n_1 \\ n_2 \end{matrix} & \begin{bmatrix} -1 & 0 & -1 \\ 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \\ & \begin{matrix} b_1 \\ b_2 \\ b_3 \end{matrix} & \end{matrix} \begin{matrix} \\ \text{node} \\ \\ \end{matrix}$$

branch (aka element)

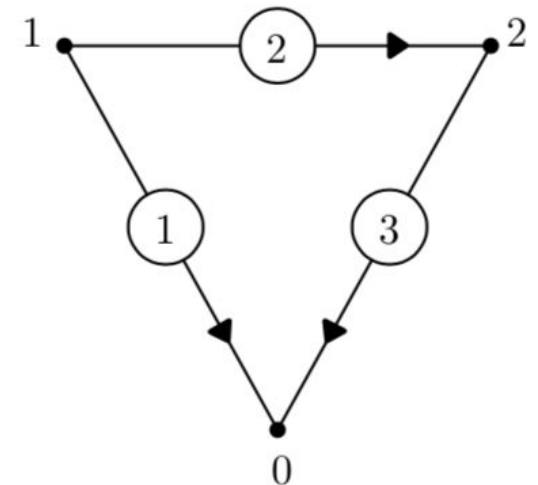
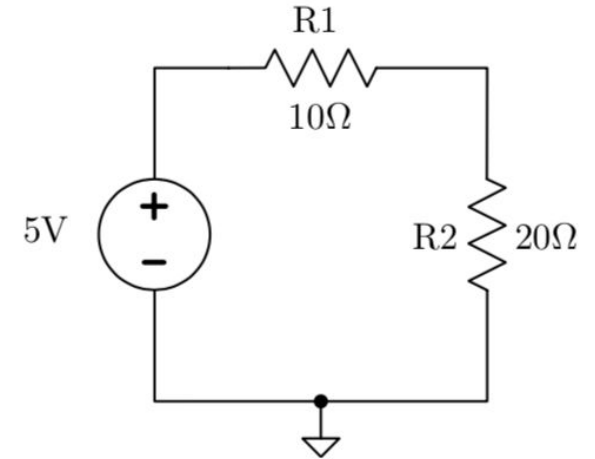


- Assume “1” is source and “-1” is destination.
- In each column, we put a “1” in the source node row and “-1” in the destination node row.

Step 2: From Netlist to Matrix



- We can further remove the row for one node (usually the ground node) to get a *reduced incidence matrix*.
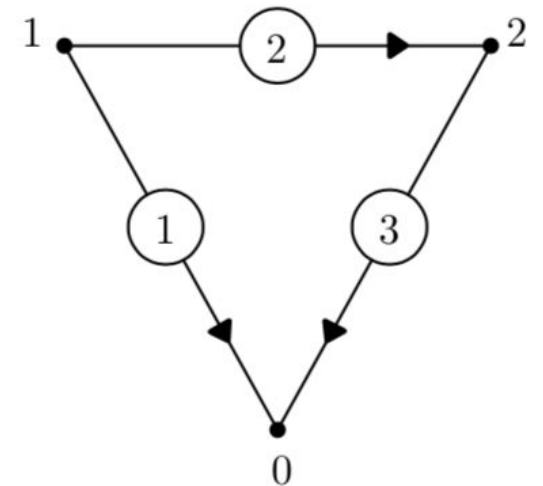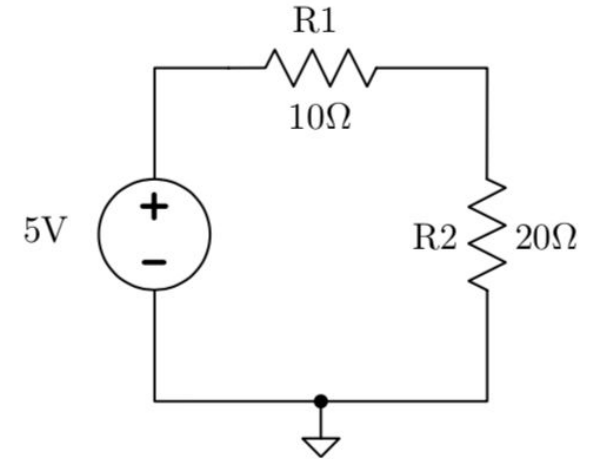
$$A_a = \begin{matrix} & \cancel{n_0} \\ n_1 & \begin{bmatrix} -1 & 0 & -1 \end{bmatrix} \\ n_2 & \begin{bmatrix} 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \end{matrix} \begin{matrix} \\ \\ b_1 \quad b_2 \quad b_3 \end{matrix} \Rightarrow A = \begin{bmatrix} 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix}$$



Step 2: From Netlist to Matrix

- **Kirchoff's Current Law (KCL):** the algebraic sum of currents that leave any node is zero.
- KCL equation for each node:
 - Assume leaving is positive and coming is negative:
 - At Node 0: branch currents i_1 and i_3 are coming, so
$$-i_1 - i_3 = 0$$
 - At Node 1: branch currents i_1 and i_2 are leaving, so
$$i_1 + i_2 = 0$$
 - At Node 2: branch current i_2 is coming, while i_3 is leaving, so
$$-i_2 + i_3 = 0$$

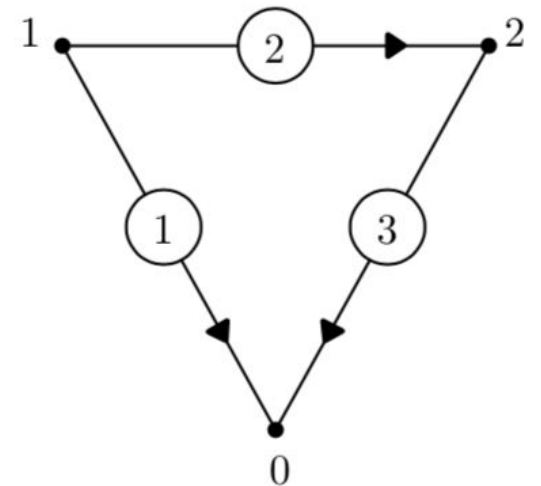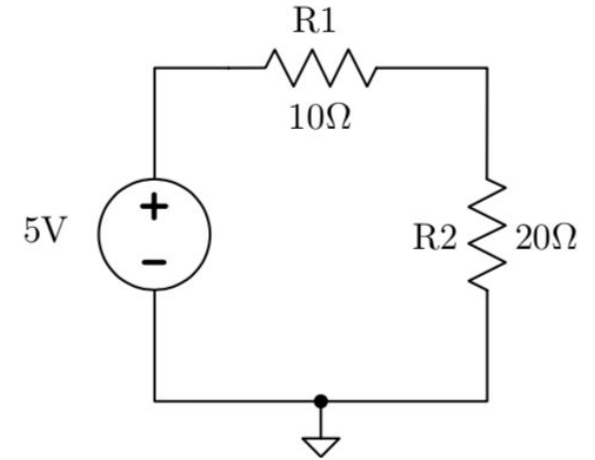

Step 2: From Netlist to Matrix

- (Cont.) Now we have:



$$-i_1 - i_3 = 0$$

$$i_1 + i_2 = 0$$

$$-i_2 + i_3 = 0$$



- Represent these equations with matrices:
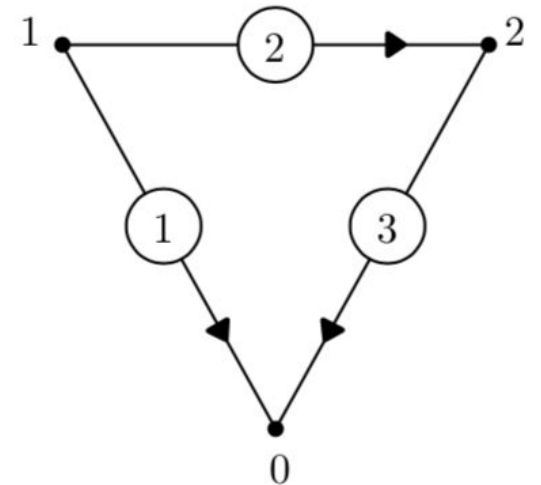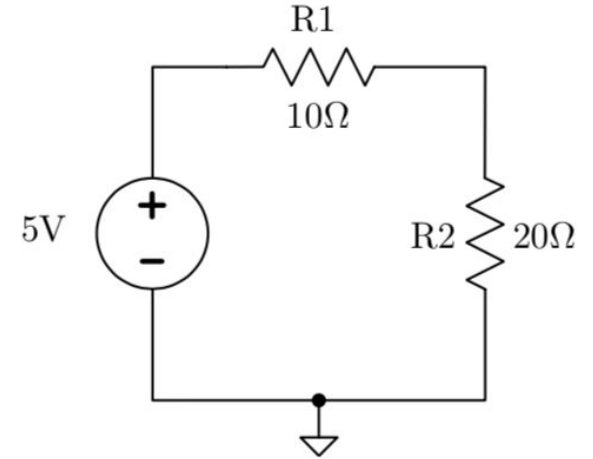
$$\begin{bmatrix} \cancel{-1} & \cancel{0} & \cancel{-1} \\ 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} \quad \Rightarrow \quad \mathbf{A}\mathbf{i} = \mathbf{0}$$



Step 2: From Netlist to Matrix

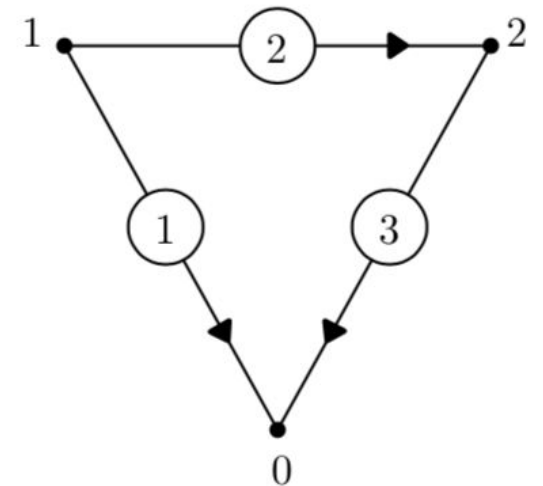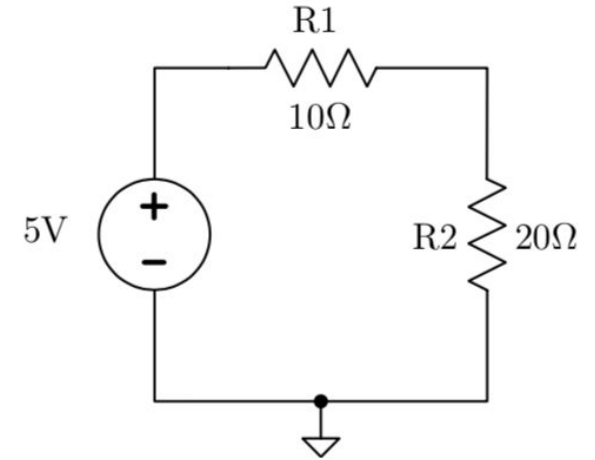- **Kirchhoff's Voltage Law (KVL):** the voltage drop between any two nodes is equal to the difference of the two node voltages.
- KVL equation for each pair of nodes:
 - Voltage drop between n0 and n1 (branch 1):
$$v_1 = e_1 - 0$$
 - Voltage drop between n1 and n2 (branch 2):
$$v_2 = e_1 - e_2$$
 - Voltage drop between n0 and n2 (branch 3):
$$v_3 = e_2 - 0$$



Step 2: From Netlist to Matrix

- (Cont.) Now we have:



$$v_1 = e_1 - 0$$

$$v_2 = e_1 - e_2$$

$$v_3 = e_2 - 0$$

- Represent these equations with matrices:
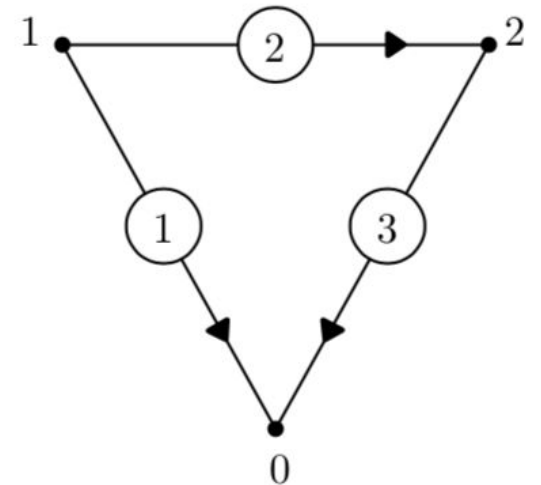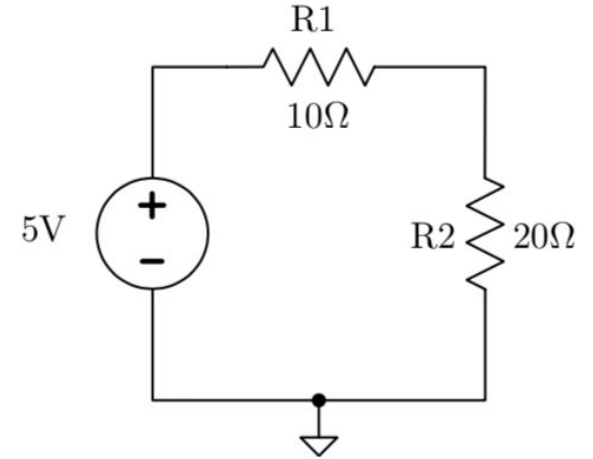
$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} \quad \Rightarrow \quad \mathbf{v} = \mathbf{A}^T \mathbf{e}$$



Step 2: From Netlist to Matrix

- Comparison between KCL and KVL:

KCL



$$\begin{bmatrix} -1 & 0 & -1 \\ 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$$A\mathbf{i} = \mathbf{0}$$

KVL

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix}$$

$$\mathbf{v} = \mathbf{A}^T \mathbf{e}$$

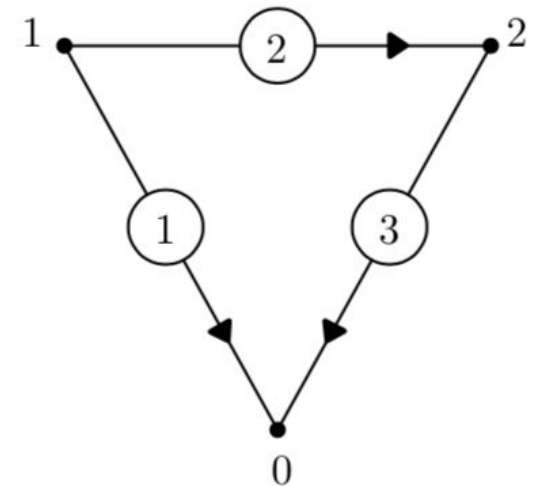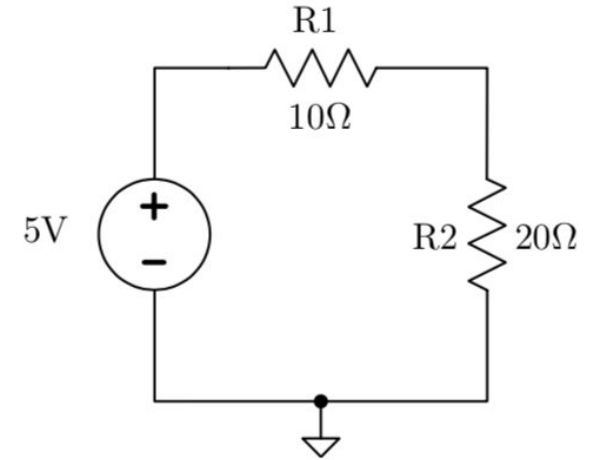

Step 2: From Netlist to Matrix



- Combine the KCL and KVL equations:

$$Ai = 0$$

$$v = A^T e$$


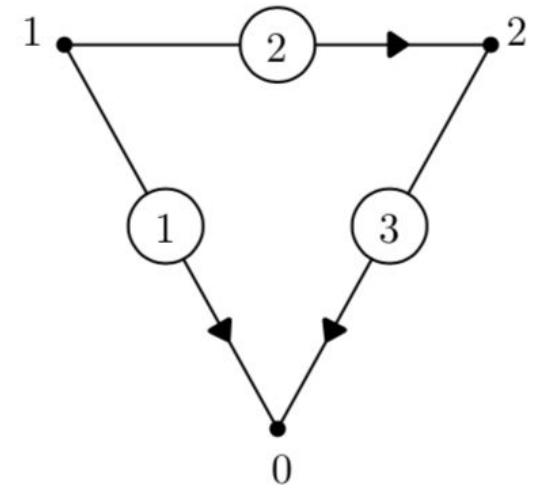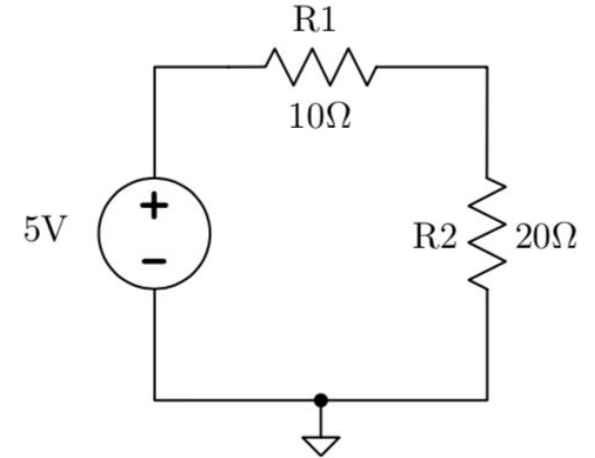
$$\begin{bmatrix} \mathbf{0} & \mathbf{0} & A \\ -A^T & \mathbf{1} & \mathbf{0} \end{bmatrix} \begin{bmatrix} e \\ v \\ i \end{bmatrix} = \begin{bmatrix} \mathbf{0} \\ \mathbf{0} \end{bmatrix}$$



Step 2: From Netlist to Matrix

- **Ohm's law:** the current through a conductor between two points is directly proportional to the voltage across the two points.



- $I = \frac{V}{R}$

- Ohm's law equation for each component:

$$v_1 = 5$$

$$v_2 = 10i_2$$

$$v_3 = 20i_3$$

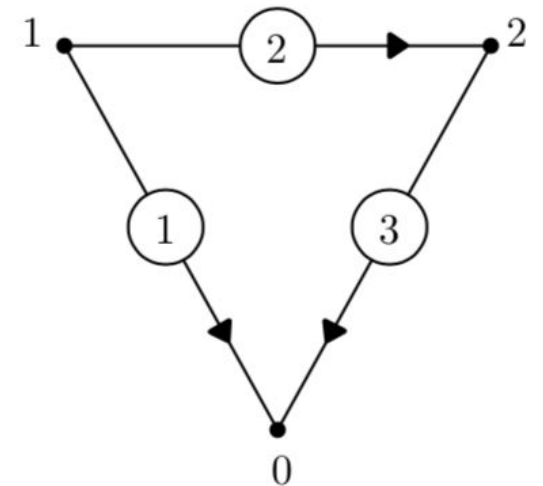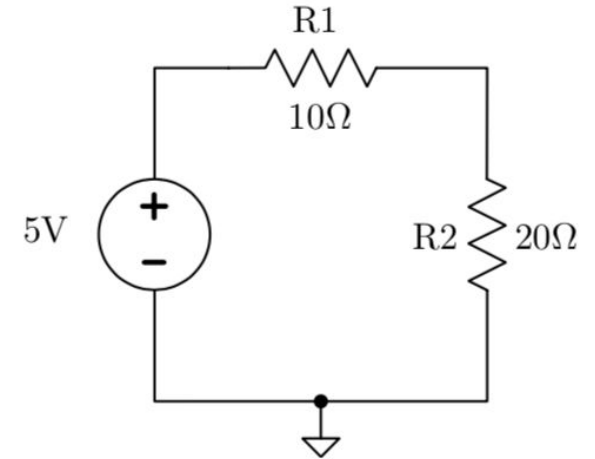

Step 2: From Netlist to Matrix

- (Continue) Represent these equations with matrices:

$$\begin{aligned} v_1 &= 5 \\ v_2 &= 10i_2 \\ v_3 &= 20i_3 \end{aligned}$$

→

$$\begin{aligned} v_1 + 0i_1 &= 5 \\ v_2 - 10i_2 &= 0 \\ v_3 - 20i_3 &= 0 \end{aligned}$$

↓ ↓ ↓
voltages currents constants

Format: $av_b + bi_b = u_s$

→

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 \\ 0 & -10 & 0 \\ 0 & 0 & -20 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

↓

$$\boxed{Mv + Ni = u_s}$$

Step 3: Calculate Unknown Parameters

- Now, what do we have?

- KCL + KVL:

$$\begin{bmatrix} \mathbf{0} & \mathbf{0} & \mathbf{A} \\ -\mathbf{A}^T & \mathbf{1} & \mathbf{0} \end{bmatrix} \begin{bmatrix} \mathbf{e} \\ \mathbf{v} \\ \mathbf{i} \end{bmatrix} = \begin{bmatrix} \mathbf{0} \\ \mathbf{0} \end{bmatrix}$$

Ohm's Law:

$$\mathbf{M}\mathbf{v} + \mathbf{N}\mathbf{i} = \mathbf{u}_s$$

- Combine all the equations to create the *combined matrix*:

$$\begin{bmatrix} \mathbf{0} & \mathbf{0} & \mathbf{A} \\ -\mathbf{A}^T & \mathbf{1} & \mathbf{0} \\ \mathbf{0} & \mathbf{M} & \mathbf{N} \end{bmatrix} \begin{bmatrix} \mathbf{e} \\ \mathbf{v} \\ \mathbf{i} \end{bmatrix} = \begin{bmatrix} \mathbf{0} \\ \mathbf{0} \\ \mathbf{u}_s \end{bmatrix} \quad \Rightarrow \quad \mathbf{T}\mathbf{w} = \mathbf{u}$$

Step 3: Calculate Unknown Parameters

$$\begin{bmatrix} \mathbf{0} & \mathbf{0} & \mathbf{A} \\ -\mathbf{A}^T & \mathbf{1} & \mathbf{0} \\ \mathbf{0} & \mathbf{M} & \mathbf{N} \end{bmatrix} \begin{bmatrix} \mathbf{e} \\ \mathbf{v} \\ \mathbf{i} \end{bmatrix} = \begin{bmatrix} \mathbf{0} \\ \mathbf{0} \\ \mathbf{u}_s \end{bmatrix}$$



Put everything we know
into the matrices

$$\left[\begin{array}{cc|ccc|ccc} 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 \\ \hline -1 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ -1 & 1 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 & 1 & 0 & 0 & 0 \\ \hline 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & -10 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & -20 \end{array} \right] \begin{bmatrix} e_1 \\ e_2 \\ v_1 \\ v_2 \\ v_3 \\ i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 5 \\ 0 \\ 0 \end{bmatrix}$$

**Final goal: calculate
e, v, and i!**

Steps Review

1. Read a netlist as input to represent a circuit
2. Use KCL, KVL and Ohm's law to construct three matrix equations
 - Construct \mathbf{A} , \mathbf{M} , \mathbf{N} , and \mathbf{u}_s to represent the netlist.
3. Combine all the matrix equations to solve all the unknown parameters (e , v , i of each part)
 - Use Gauss Elimination, LU Factorization, etc.
4. Output voltages and currents

Bigger Example

- Input:
 - V1 1 0 6
 - R1 1 2 6
 - R2 2 0 3.33
 - R3 2 3 3
 - R4 3 0 11
 - R5 3 4 4
 - R6 4 0 7
 - R7 4 5 7
 - R8 5 0 7

Bigger Example

- $\mathbf{A} = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 \end{bmatrix}$

- $\mathbf{M} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$

Input:

V1 1 0 6

R1 1 2 6

R2 2 0 3.33

R3 2 3 3

R4 3 0 11

R5 3 4 4

R6 4 0 7

R7 4 5 7

R8 5 0 7

Bigger Example

•	N =									u_s =		Input:
	0	0	0	0	0	0	0	0	0	6		V1 1 0 6
	0	-6	0	0	0	0	0	0	0	0		R1 1 2 6
	0	0	-3.33	0	0	0	0	0	0	0		R2 2 0 3.33
	0	0	0	-3	0	0	0	0	0	0		R3 2 3 3
	0	0	0	0	-11	0	0	0	0	0		R4 3 0 11
	0	0	0	0	0	-4	0	0	0	0		R5 3 4 4
	0	0	0	0	0	0	-7	0	0	0		R6 4 0 7
	0	0	0	0	0	0	0	-7	0	0		R7 4 5 7
	0	0	0	0	0	0	0	0	-7	0		R8 5 0 7

Excursion 1 Quiz